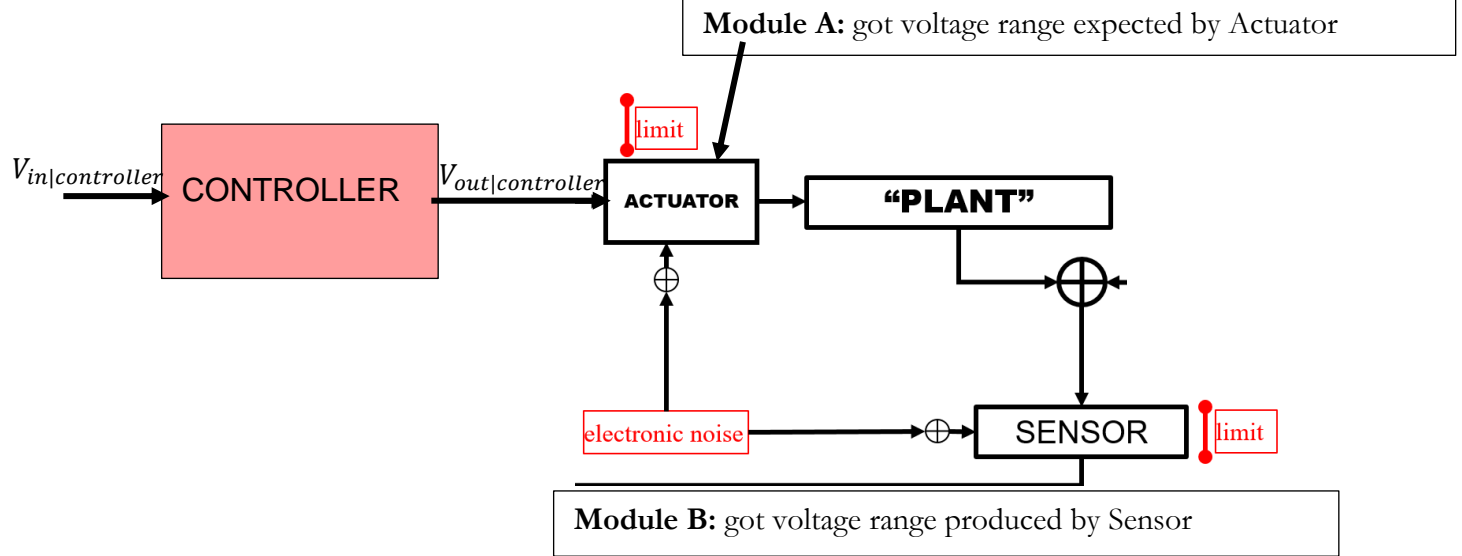


PH233 End-semester exam Module C: Controller

From Modules A and B we have a clear idea of the range of voltages coming from the sensor, and the range of voltages to be driven into the actuator as shown in Fig 1

Fig 1: Progress so far from Modules A + B: we have the plant, now we build the controller



In this module, we will build and test the highlighted controller module in Fig 1

Since $V_{out|sensor}$ and $V_{in|actuator}$ ranges are known, we are now ready to implement the mathematical feedback equation:

$$V_{out|controller} = K_p e(t) + K_I \int_0^t e(\tau) d\tau + K_D \frac{de}{dt}$$

in terms of real voltage signals between opamp based blocks

For this assignment, we simplify the controller by dropping the latter 2 terms and implementing only the proportional term:

$$V_{out|controller} = K_p e(t) \dots \text{Equation (1)}$$

Though very simple, controller based on equation 1 has major drawbacks for our breadboard feedback control system:

$V_{out|controller}$ can be positive or negative depending upon sign of $e(t)$. However, our actuator (LED) requires positive drive voltage (0 – 4V as tested in Module A). Hence $V_{out|controller} \rightarrow V_{in|actuator}$ needs to be positive definite

If we don't make provision for an offset voltage, consider the case when $e(t) \rightarrow 0$: $V_{out|controller} = 0$, thus turning-off the LED. No light incident on the sensor will increase $e(t)$ to maximum pushing $V_{out|controller}$ to max driving the LED back to full brightness! This cycle continues and the controller will oscillate

Hence, we need to modify the controller output equation by adding an offset

$$V_{out|controller} = K_p e(t) + V_{Offset} \dots\dots \text{Equation (2)}$$

Where V_{Offset} is generally set to half the range of $V_{in|actuator}$.

Use **INVERTING** configuration opamps for both the following questions C.1 and C.2. To keep the two terms in Equation 2 independent, use one opamp to implement $K_p e(t)$ and a second opamp to add V_{offset}

C.1) P controller $K_p e(t)$

10


This is simply an inverting opamp gain configuration whose gain corresponds to the proportional constant K_p

Design and build an inverting gain opamp. Set the gain with a tunable resistor ratio (use a 10k Ω potentiometer in the feedback loop to set the gain)

Test the functioning of your P block and tune its K_p gain by injecting various DC voltages $V_{in|controller} = -0.2V$ to $0.2V$ to make sure it does not saturate the limits of $V_{out|controller}$. Assume that this is the worst case error imbalance you expect to see when you close the feedback loop.


Circuit design and simulation (LTSpice)

5

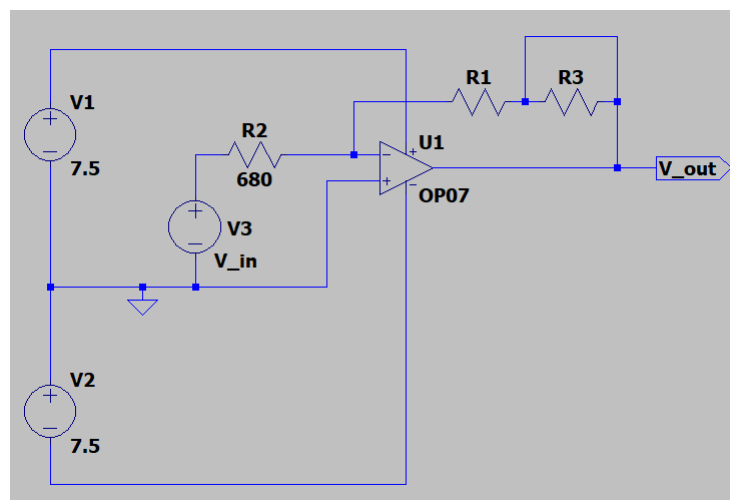

(NOTE: $V_1 = V_2 = 7.5V$ due to draining of my battery after prolonged use. Hence, used the same value in the simulation)

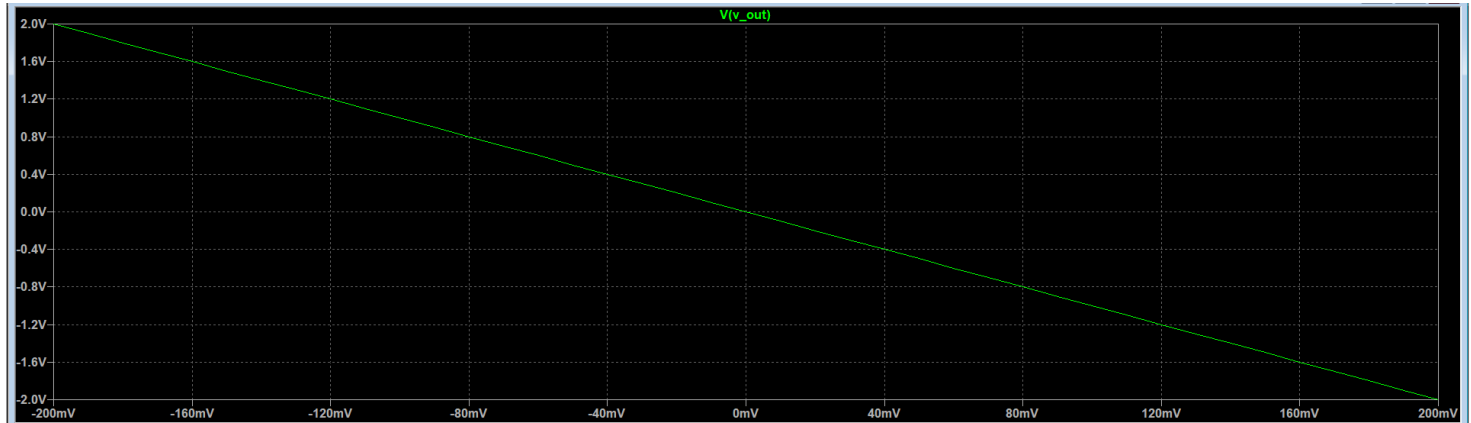In the above circuit, R_1 and R_3 correspond to the potentiometer, and V_{in} ranges from $-0.2V$ to $+0.2V$.




For obtaining the plot above with gain = 10, $R_2 = 6.8k\Omega$ and $R_3 = 3.2k\Omega$. A DC sweep analysis on V_3 with range $-0.2V$ to $+0.2V$ generates the above plot.


Photos of built-up circuit tested with worst case DC input voltages of $-0.2V$ and $+0.2V$ and corresponding output voltages at $K_p = 10$ (measure with DMM)


5

$V_{IN} = +0.2V$

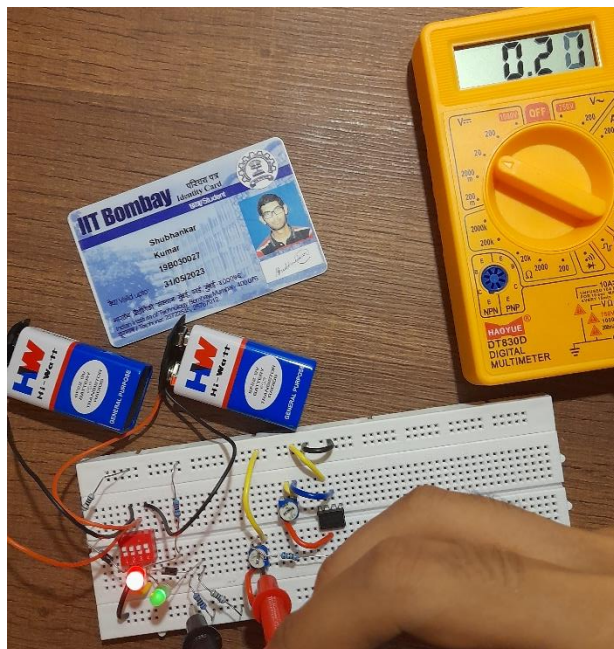

$V_{OUT} = -2.06V$

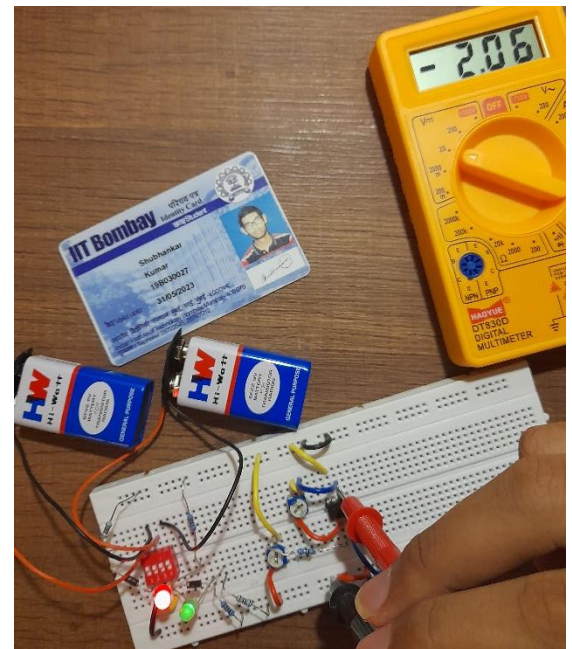

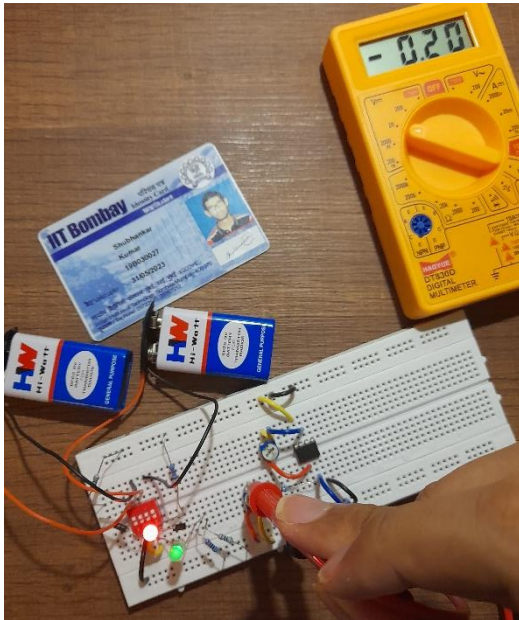

$$V_{IN} = -0.2V$$



$$V_{OUT} = 2.14V$$

C.2) Offset to be added to P control + V_{adjust} 10

The keyword here is that you need a **summing** amplifier. $K_P e(t)$ is summed with an adjustable DC voltage.

$$V_{out|controller} = K_P e(t) + V_{adjust} \quad \dots \text{Equation (2)}$$


Notice that the gain K_P in the feedback controller (Equation 1) is positive by definition.

Due to the TWO inverting stages used in the above questions C.1 and C.2, the net gain of your P controller will be positive Each opamp is setup up for inverting operation. So $(-1) \times (-1)$ the net gain of the controller comes out positive.


The advantage of using two opamps is that it allows you to keep the two terms in Eqn 2 independent

LTSpice Circuit design and simulation adding two DC voltage levels

5

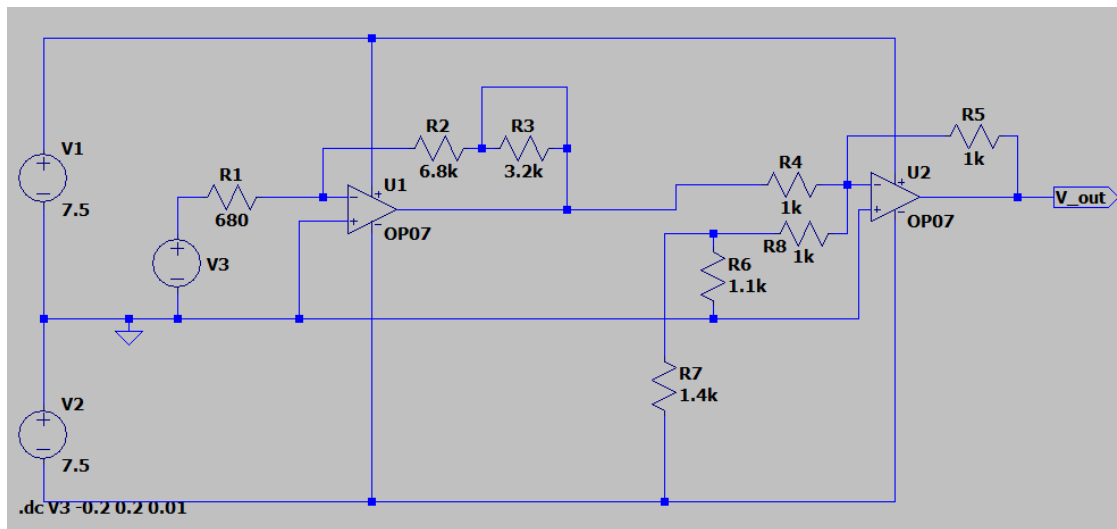


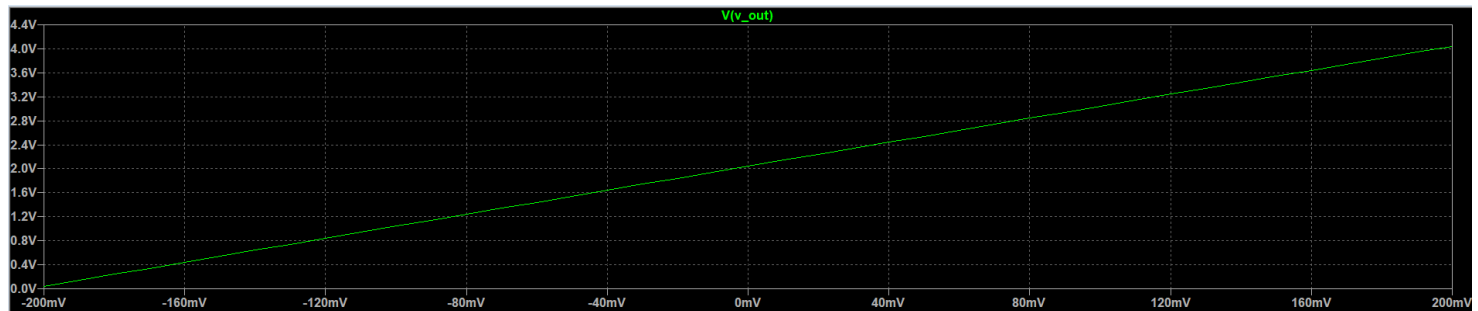In the above circuit, R6 and R7 are chosen such that $V_{\text{junction}} = -2\text{V}$




We see that for $V_{\text{IN}} = -0.2\text{V}$, the output from the first op amp will be $+2\text{V}$. This is added with $V_{\text{adjust}} = -2\text{V}$, giving 0V as the output from the second op amp. In a similar way, we get $+4\text{V}$ as the final output when $V_{\text{IN}} = +0.2\text{V}$

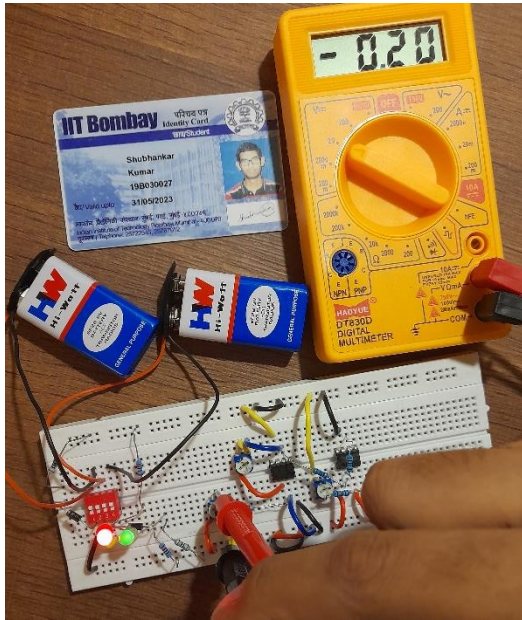Circuit demo: Connect the summing amplifier on your breadboard. Measure with DMM a DC voltage $+2\text{V}$ being summed to each of the $K_P \times (\pm 0.2\text{V})$ cases checked in question C.1




$$V_{IN} = -0.2V$$

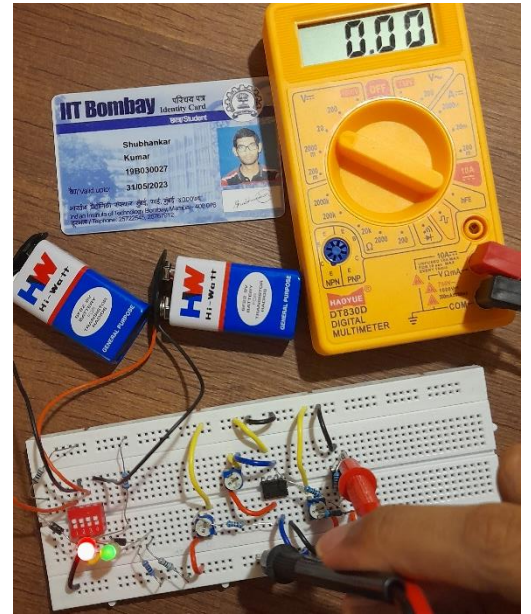

$$V_{OUT} = 0V$$



$$V_{IN} = +0.2V$$

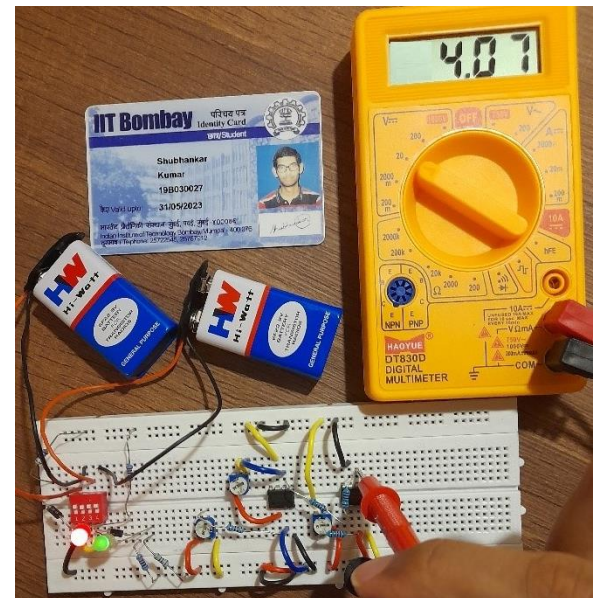

$$V_{OUT} = 4.07V$$