

Lab 3.2: Putting opamps to 'gainful' use [POSITIVE Feedback]

Conceptual introduction

The prototype design for an opamp circuit using positive feedback is shown below in Fig 1

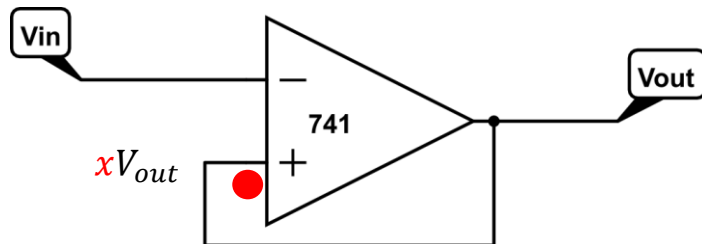


Fig 1: Prototype showing essential features of a positive feedback circuit. Fraction xV_{out} is send as feedback to the V_+ terminal

The two defining features of a positive feedback circuit are:

- 1) feedback signal is **always** applied to the V_+ terminal
- 2) V_{out} can have only two values - $+V_{sat}$ *or* $-V_{sat}$: these are the two states of the output – we will refer to the output ‘switching’ between these two states. V_{sat} is the maximum saturation voltage of the opamp output, usually a volt or so less than V_{CC}

The two Golden Rules of opamp design are obviously still applicable and all analysis is done on the basis of those two rules.

1) Circuit design

Problem statement:

What we DON'T want: Opamp running open-loop acts a comparator.

In Fig 1, consider what happens when the circuit in Fig 1 does not have the feedback loop in place. If $x = 0$ (i.e. V_+ is set to GND (and disconnected from V_{out} , breaking the feedback connection) then, V_{out} will switch states when V_{in} transitions from $V_{in} < 0$ to $V_{in} > 0$ and vice versa. However, as we know voltages are always noisy! So a small noise fluctuation in V_{in} around transition threshold will cause the output to switch multiple times.

With your kit's current battery state (maybe much less than 9V!) check the V_{sat} values you get with opamp open-loop comparator – most of the calculations below will depend on the numerimcal V_{sat}

WHAT WE WANT: Design a circuit that is called a “Schmitt Trigger”

The problem with noisy V_{in} and the desired solution for behavior of V_{out} is shown in Fig 2

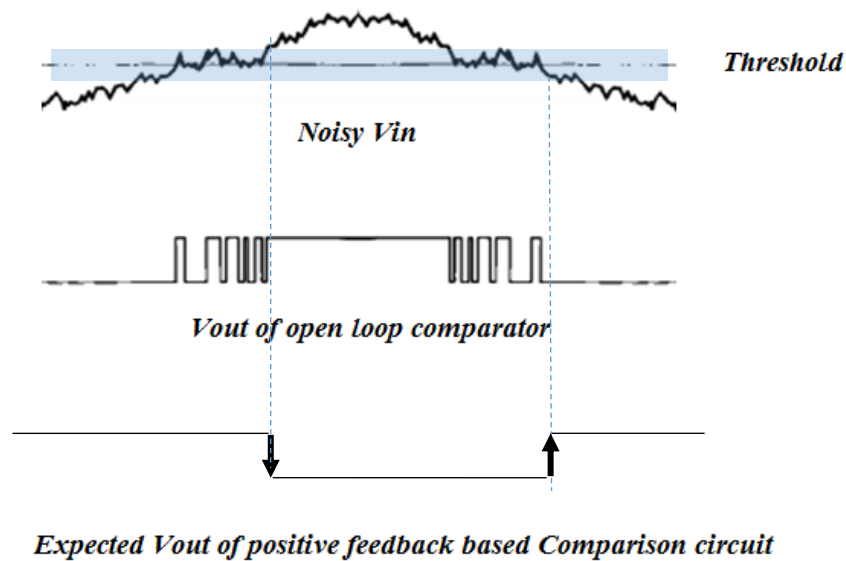


Fig 2: V_{out} of open loop comparator switches many times as noisy V_{in} crosses threshold.

OBJECTIVE: Should be able to set a specified value of threshold voltage V_T and have a specified safety 'noise' band around the threshold (marked as blue shaded box):

Required circuit: V_{out} must switch only when V_{in} exits that safety band.

Note: Timing & logic of the transitions highlighted above are caused by the intrinsic structure of our **inverting** Schmitt trigger.

Design specification:

As per Figures 1 and 2, design a positive feedback circuit using the LM741 such that:

- 1) Threshold Voltage $V_T = 2V$
- 2) Noise band allowed around V_T is $\pm 0.3V$
- 3) Use regular opamp power supply setup as earlier $\pm V_{CC} \sim \pm 8V$ don't forget the power supply bypass caps!

Hints for design:

- a) As in negative feedback the fraction xV_{out} is set by a resistor divider. However, now our analysis is constrained by V_{out} being stuck to $\pm V_{sat}$ and having to set two bounds on the comparison :
both $2V + 0.3V$ and $2V - 0.3V$
For simplicity we have asked for a symmetrical noise band around V_T . In principle it is possible to set different lower and upper bounds around V_T
- b) You will find **THREE** resistors are required instead of two as used in the negative feedback case.
- c) Generally, such a circuit is called a 'Schmitt Trigger'

Solution to Question 1)

5

Put a sketch of your Schmitt Trigger design here labelling the resistors and the design calculation equations that fulfill the required specifications.

(can be photo of hand-drawn sketch). Equations must be properly formatted


$$\text{We have, } V_T = \frac{R}{R_3} V_{CC} \pm \frac{R}{R_1} V_{sat}$$

$$\text{Where } R = R_1 || R_2 || R_3 \text{ and } V_{CC} = V_{sat} = 8V$$

$$\text{We equate } \frac{R}{R_3} V_{CC} = 2V \text{ and } \frac{R}{R_1} V_{sat} = 0.3V$$

$$\text{On solving these, we get } R_1 = \frac{20}{3} R_3 \text{ and } R_2 = \frac{20}{57} R_3$$

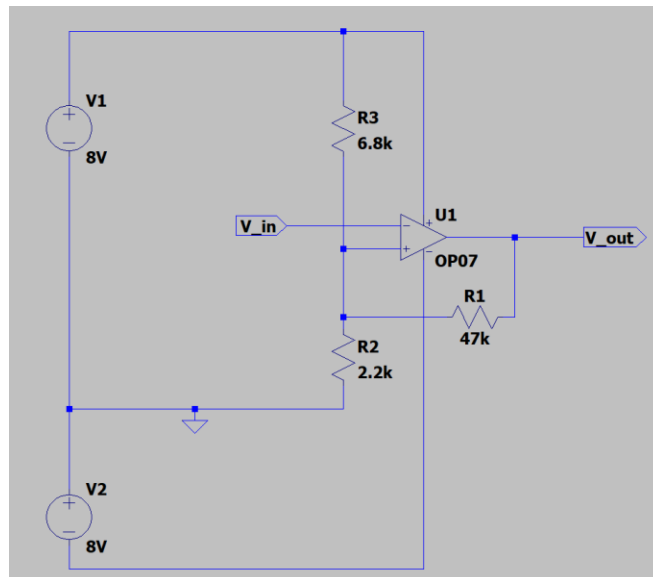R_3 can be chosen to be $6.8k\Omega$. Therefore, $R_1 = 47k\Omega$ and $R_2 = 2.2k\Omega$



2) Simulation

5

Simulate the circuit in LTSpice. For V_{in} Use the full-scale output of your standard square waveform from FG's collector of transistor Q3. Normally, the square wave output of the FG swings 0V to slightly less than V_{CC} .


Simulation will give a very fast transition across the threshold voltage. But note that in the next question, when you do the circuit test the actual V_{CC} may be much lesser, and V_{in} will be quite a bit noisier!

Circuit diagram **2 marks**


Plot of V_{out} & V_+ (time domain) **1 mark**

Plot of V_{out} v/s V_{in} **2 marks (notice the hysteresis behavior!)**


Circuit Diagram

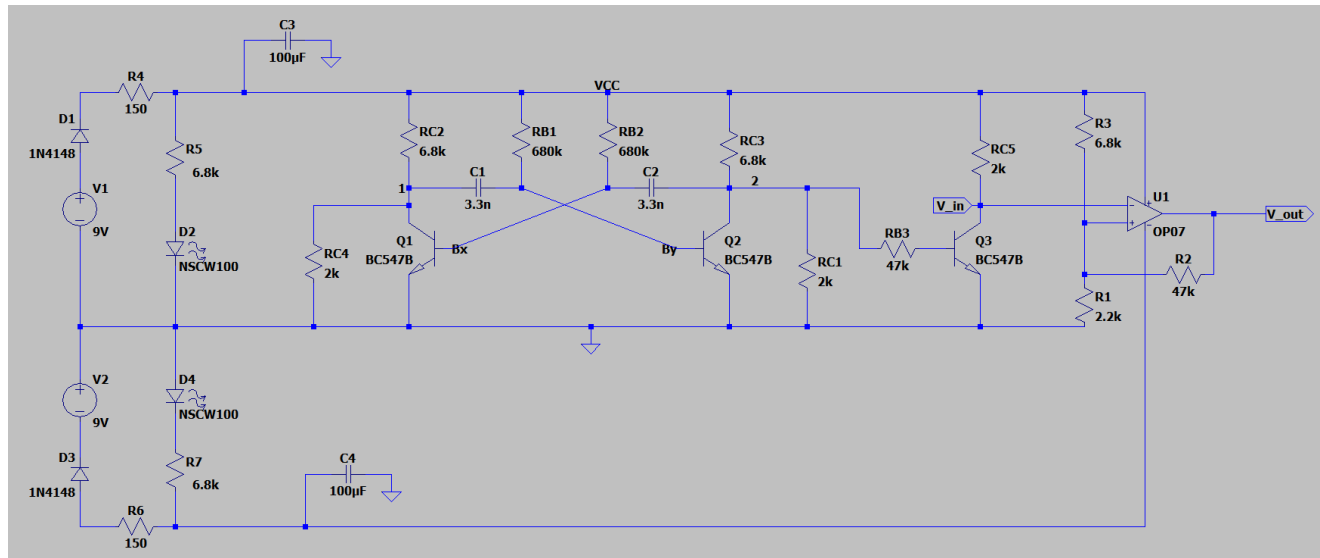


V_{out} vs time

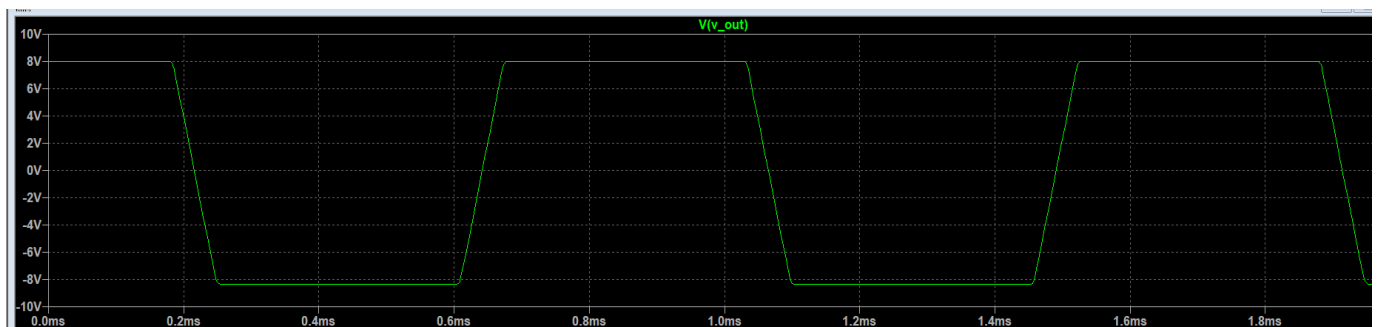

V₊ vs time

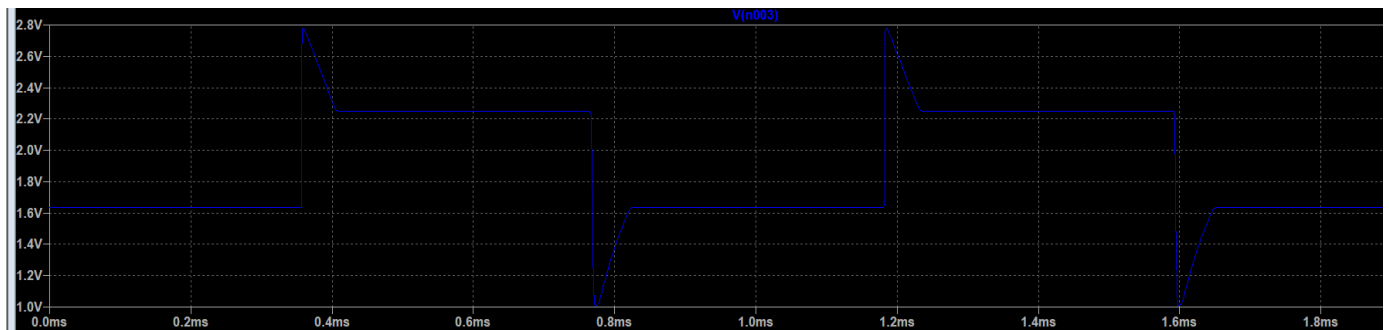

V_{out} vs V_{in}

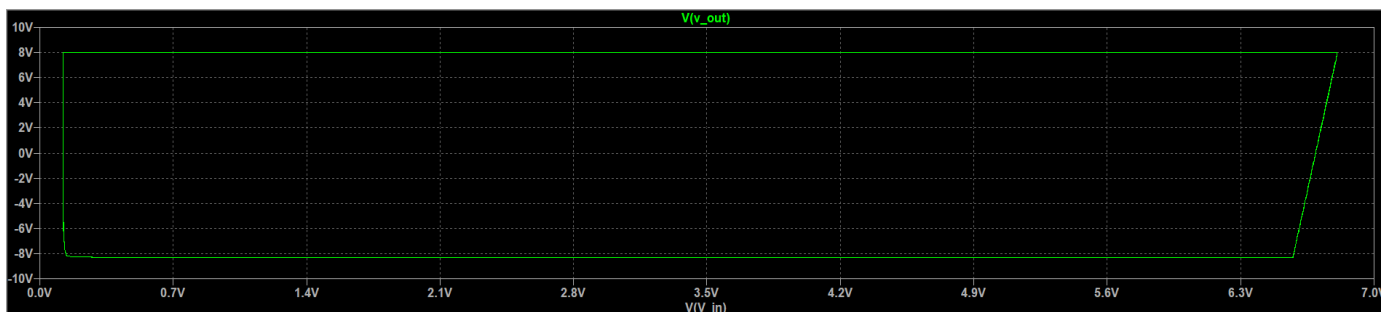




3) Circuit test – electrical voltages

5

Build the Schmitt trigger circuit designed and simulated on your breadboard.

Do a photogenic demo of your V_+ and the V_{out} of your Schmitt trigger. Label each photo to distinguish which is which.

Use the full scale square wave output from FG as V_{in}

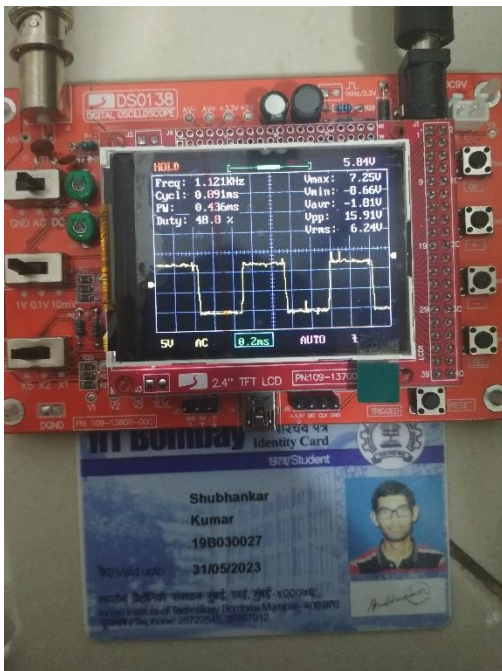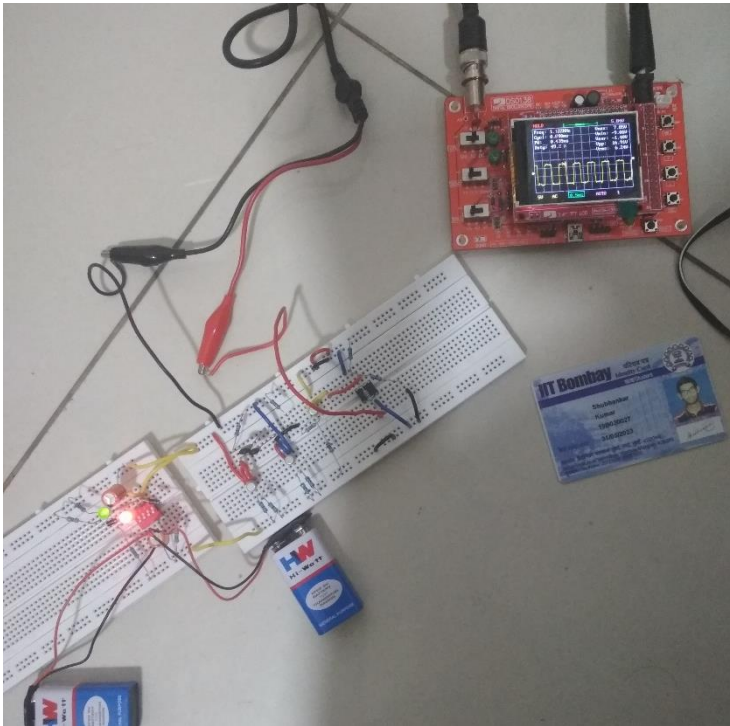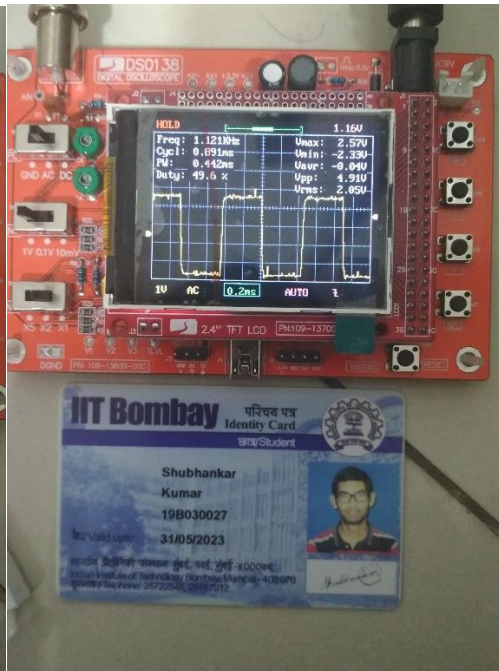
 V_{out}

 V_+



4) Circuit test – noisy light intensity measurement

10


Now we would like to test the Schmitt trigger with a realistic, noisy sensor voltage input.

Sensor: Setup the photo-transistor in your kit as a light detector. With the base left unconnected, the voltage obtained at the emitter is proportional to the light incident on the device

Light source: Use an LED connected to the FG output with a suitable series resistor to provide a variable light intensity to your sensor photo-transistor. Note that the LED and photo-transistor must be mounted facing each other on the breadboard as close to each other as possible. The LED has $\approx 60^\circ$ cone of light emission and the phototransistor also has maximum sensitivity within a 60° cone as shown below.

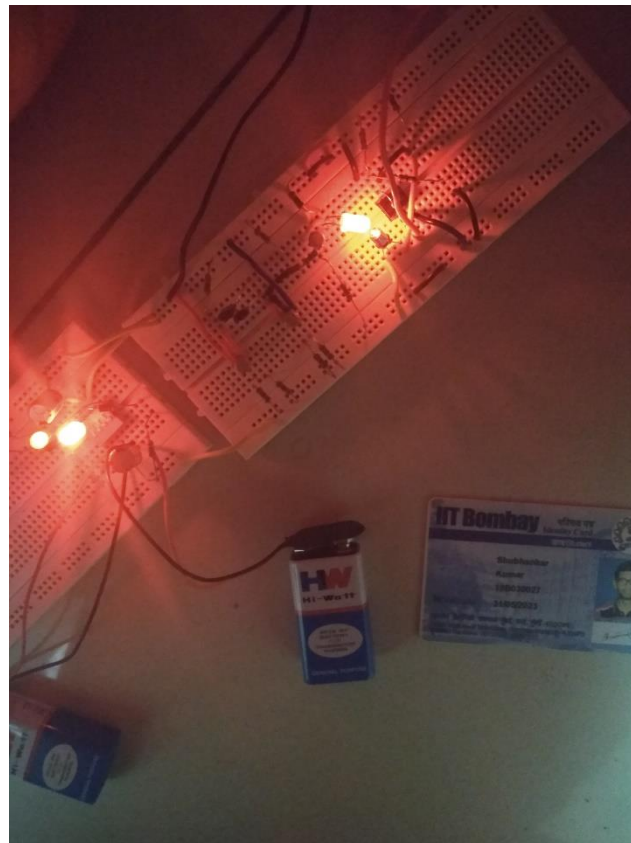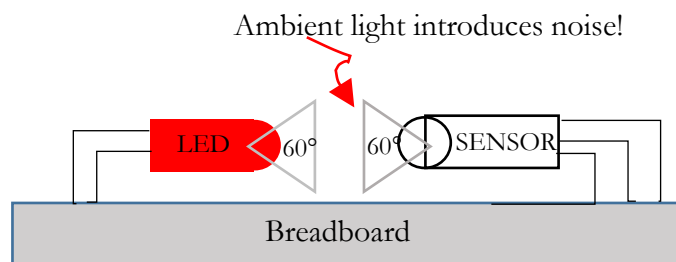

(next page)

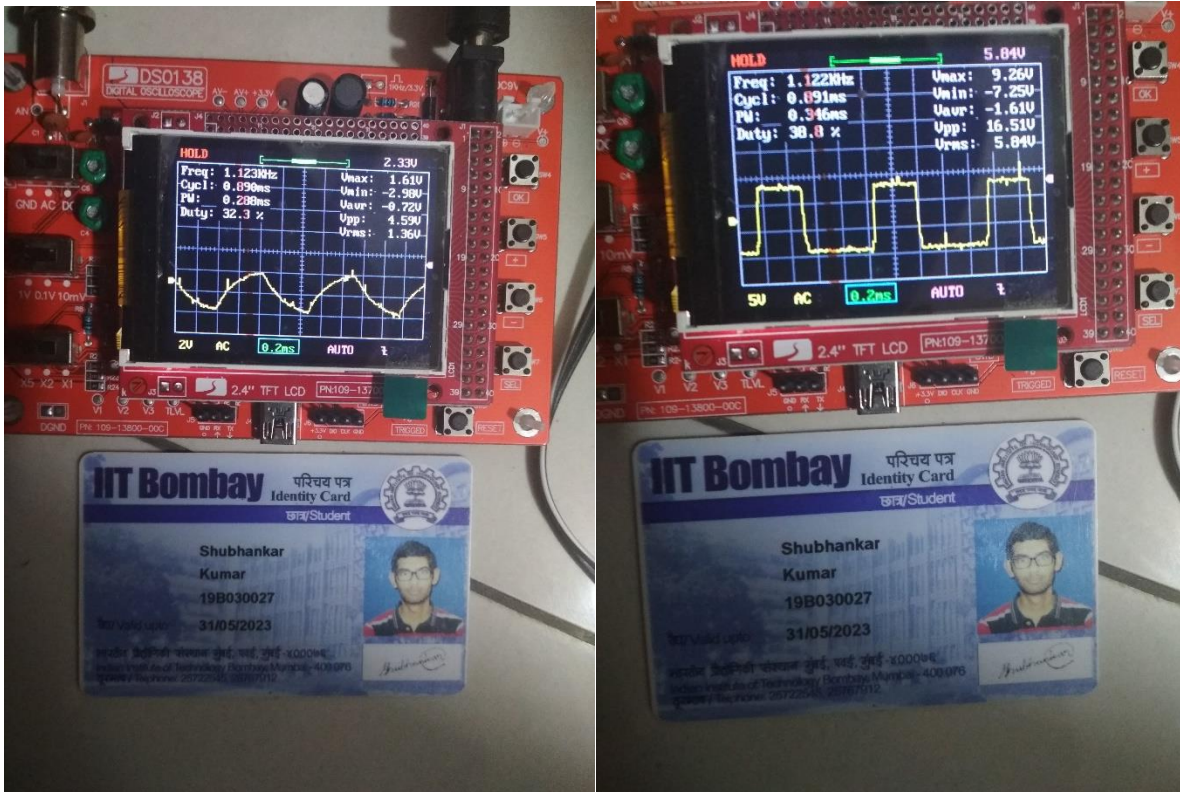 V_{in} V_{out}

We observe that the voltage waveform from the phototransistor happens to be a sawtooth wave. The output waveform from the op amp due to the Schmitt trigger will be a square wave (as shown in the right figure).