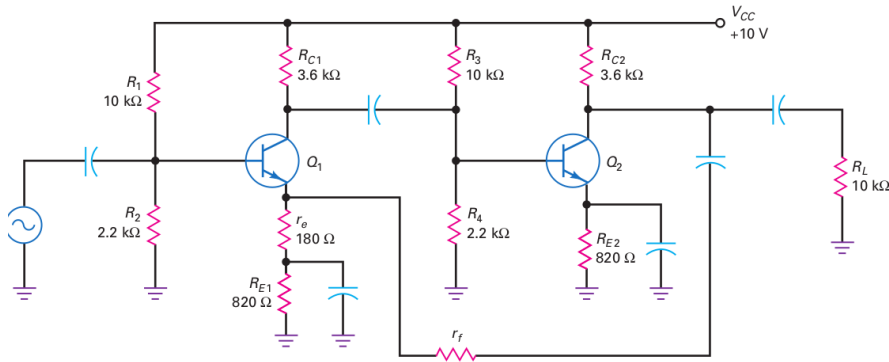



## Amplifier Tutorial Sheet

**Q1.** The two stage CE amplifier in the figure has **feedback** from the second stage




to the first stage. Obtain an expression for the AC voltage  $v_e$  at the emitter of transistor  $Q_1$ , in terms of the external emitter resistance  $r_e$ , the feedback resistance  $r_f$  and  $v_{out}$ , the AC voltage across  $R_L$ . Such an amplifier has variable gain, if  $r_f$  is a variable resistor. What should be range of  $r_f$ , if the voltage gain of this amplifier is to be in the range  $10 - 100$ .

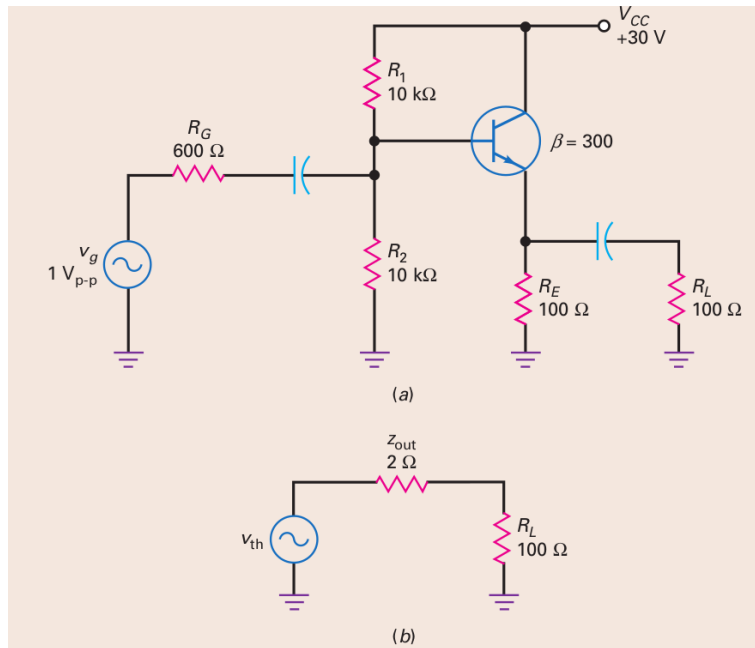**Q2.** Calculate the input impedance of the CC amplifier in the above circuit and




$v_{out}/v_g$ , where  $v_{out}$  is the voltage across the  $100\Omega$  load resistor.

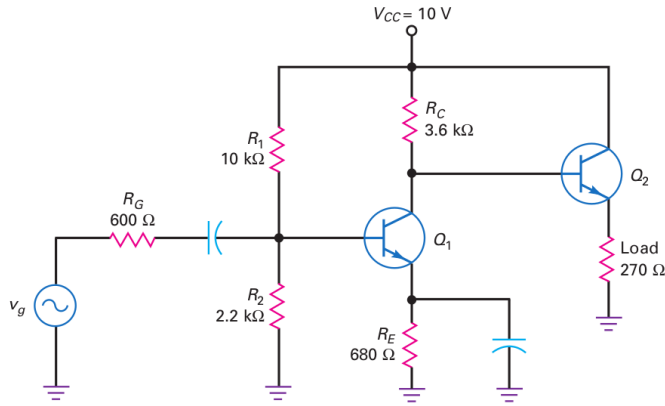**Q3.** Calculat the input impedance, output impedance and the net voltage gain




$v_{out}/v_g$  for the CE-CC cascade amplifier. The output voltage  $v_{out}$  is the AC voltage across the load resistor  $270\Omega$ .

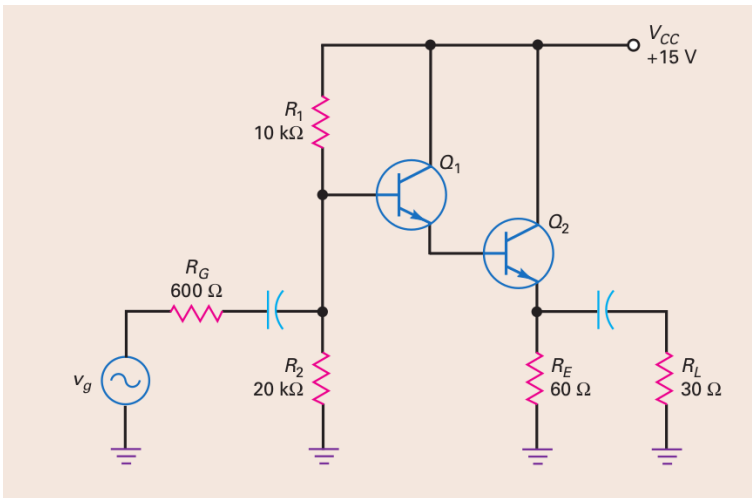**Q4.** Calculate the input impedance, output impedance and the ratio  $v_{out}/v_g$ , of




this CC amplifier with a Darlington pair, where  $v_{out}$  is the voltage across the load resistor  $R_L$ .

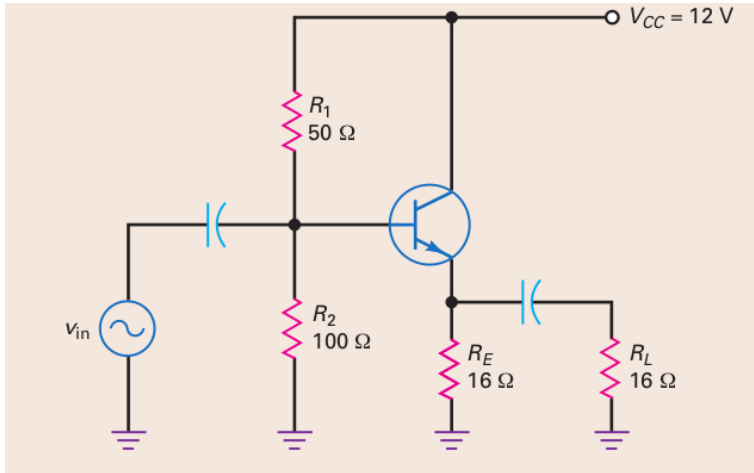**Q5.** Analyse the large signal operation of the CC amplifier in the above figure and



obtain its AC output compliance.

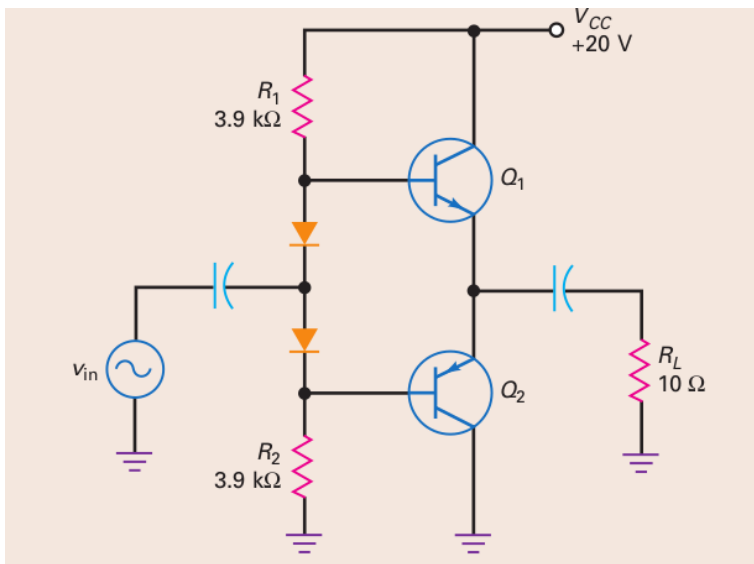**Q6.** Calculate the quiescent collector current for the push-pull amplifier in the above



circuit. What is the DC power dissipation? What is the maximum AC output power possible?