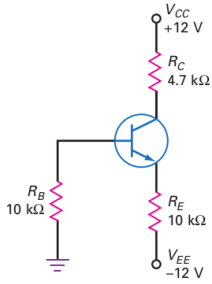


## Transistor Tutorial Sheet


**Q1.** The figure above shows a biasing scheme with two power supplies with voltage



$\pm 12$  V. Calculate  $I_C$  and  $V_{CE}$  for the transistor.


*Hint:* There are two ways to approach this problem: (a) Assume that  $I_B$  is so very small that it can be set equal to zero, figure out  $V_B$  and solve the problem. (b) Assume that the transistor has  $\beta_{dc} = 100$ , use Kirchhoff's Voltage law and solve the problem. Do the problem both ways and compare the answers.

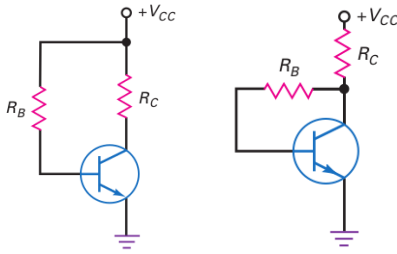**Q2.** In the above two circuits, take  $R_B = 200\text{ k}\Omega$  and  $R_C = 1\text{ k}\Omega$ . For each circuit,




calculate  $I_C$  when (a)  $\beta_{dc} = 100$  and when (b)  $\beta_{dc} = 300$ . Why is  $I_C$  in the second circuit less sensitive to  $\beta_{dc}$  compared to the first circuit?

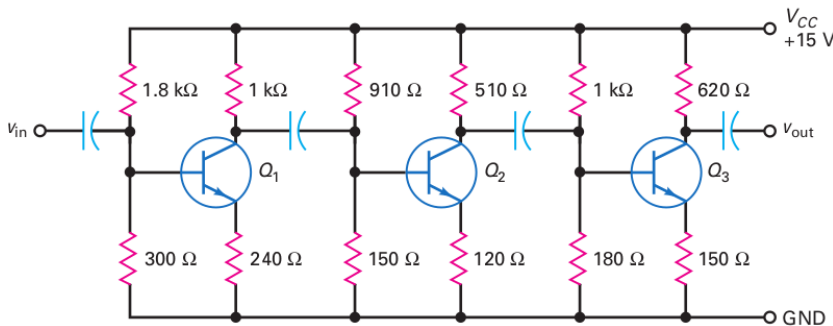**Q3.** Calculate  $I_C$  and  $V_{CE}$  for each of the three transistors in the circuit.




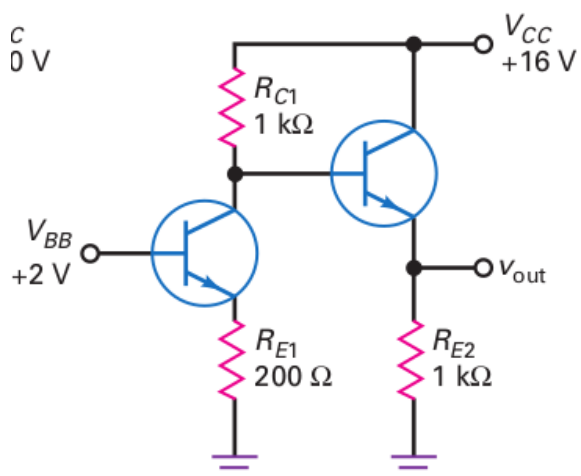**Q4.** What is the voltage  $v_{out}$  in the above circuit?




*Note:* The  $v_{out}$  in this problem is a DC voltage. So, the language in this problem violates the notation principle mentioned in class on 15th.

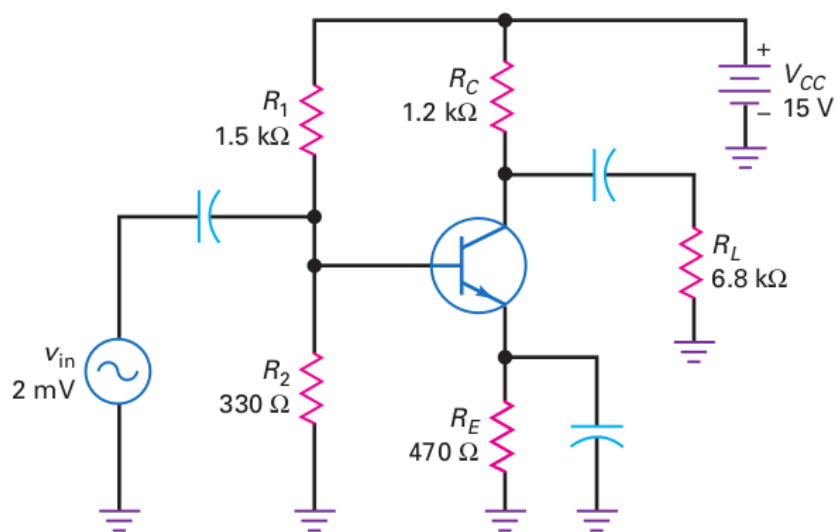**Q5.** Calculate the AC voltage gain for the CE amplifier circuit given below.




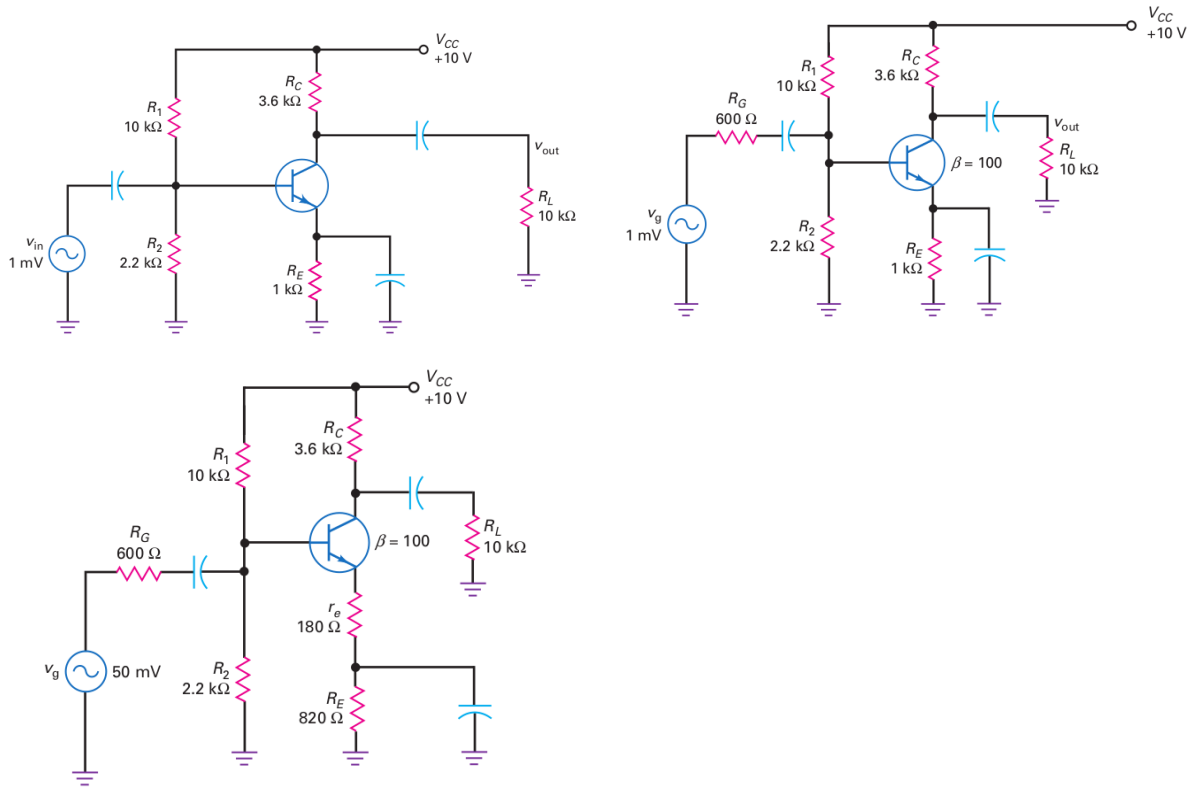**Q6.** The three circuits below have the same VDB and same  $R_L$ . But they have



small differences. The first one is an idealized circuit, the second one has a source resistance  $R_G$  and in the third one, the emitter resistance is split into  $(180+820)$ . Let  $v_{out}$  be the AC voltage across the load resistor  $R_L$ . Calculate the AC gain  $v_{out}/v_{in}$  for each of the circuits.

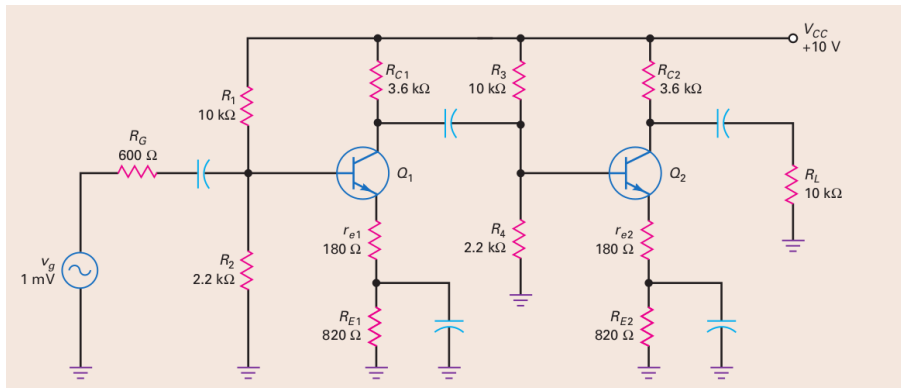**Q7.** Calculate the net voltage gain  $v_{out}/v_{in}$  for the two-stage CE amplifier in the



above circuit.  $v_{out}$  is the voltage across the load resistor  $R_L$ .