
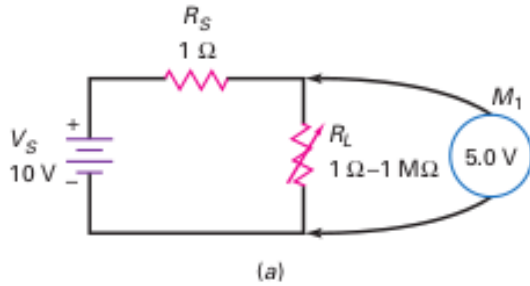


## OpAmp Tutorial Sheet

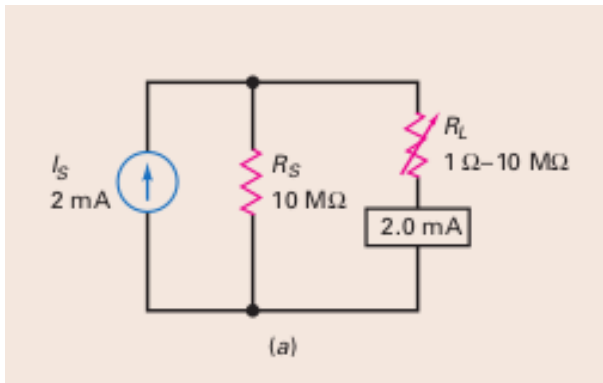**Q1.** In the above figures, we see a voltage source with a source resistance connected




to a load. In the case of the case of the voltage source, the voltage across the load is  $v_{out} = [R_L / (R_S + R_L)] * v_s$ . We have  $v_{out} = v_s$ , when the load is open (i.e.  $R_L \rightarrow \infty$ ) and  $v_{out} = v_s/2$  when  $R_L = R_S$ . We used this fact to figure out the closed loop output impedance of VCVS in the class. We can use a similar argument with current source also.



The above figure shows a current source with a source resistance  $R_S$  in parallel and a load resistance  $R_L$ . Part of the current goes through  $R_S$  and part through  $R_L$ . Obtain an expression for the current through the load  $i_L$ , in terms of  $i$ ,  $R_S$  and  $R_L$ . It is straight-forward to see that  $i_L(R_L = R_S) = i_L(R_L = 0)/2$ . We can use this fact to obtain the output resistance on VCCS

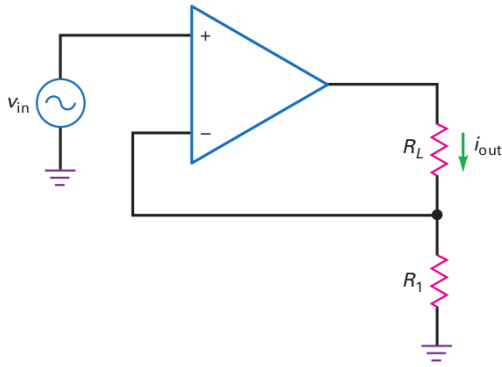**Q2.** For the Voltage Controlled Current Source, in the figure above, show that




•

$$i_L = \frac{1}{R_1 + \frac{R_1 + R_L}{A_{VOL}}} v_{in} \approx \frac{1}{R_1} v_{in},$$

that is, the load current depends purely on  $v_{in}$  and is independent of  $R_L$  and  $A_{VOL}$ .

- $z_{in(CL)} = (1 + A_{VOL}B)R_{in}$ , where  $B = R_1/(R_L + R_1)$ .
- $z_{out(CL)} = (1 + A_{VOL})R_1$ .

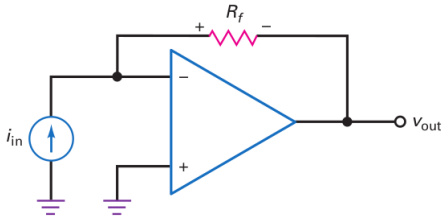**Q3.** For the Current Controlled Voltage Source (CCVS) in the figure above, show



that


•

$$v_{out} = -\frac{A_{VOL}}{1 + A_{VOL}} R_f i_{in} \approx -R_f i_{in},$$

that is, the output voltage depends purely on input current.


- $z_{in(CL)} = R_f/(1 + A_{VOL})$ .
- $z_{out(CL)} = R_{out}/(1 + A_{VOL})$ .

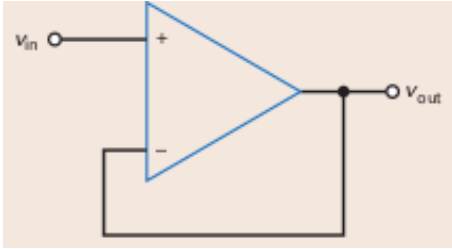**Q4.** It is straight-forward to see that, in the above circuit,  $v_{out} = v_{in}$ . What, then,




is the purpose of the OpAmp?

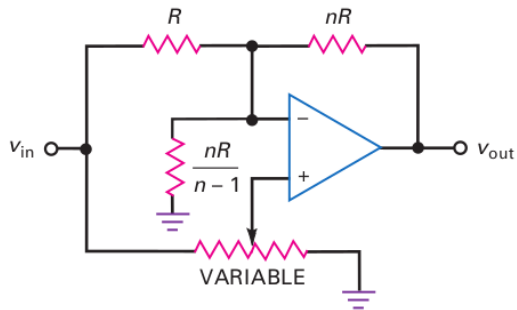**Q5.** Show that, in the figure above, the voltage gain varies from  $-n$  to  $+n$ , as the




contact of the variable resistor is moved from the right end to the left end.

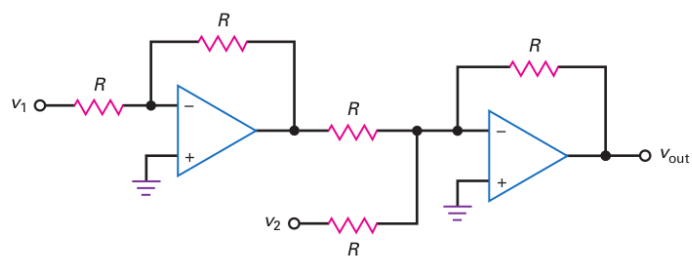**Q6.** Obtain the relation between  $v_{out}$ ,  $v_1$  and  $v_2$ .



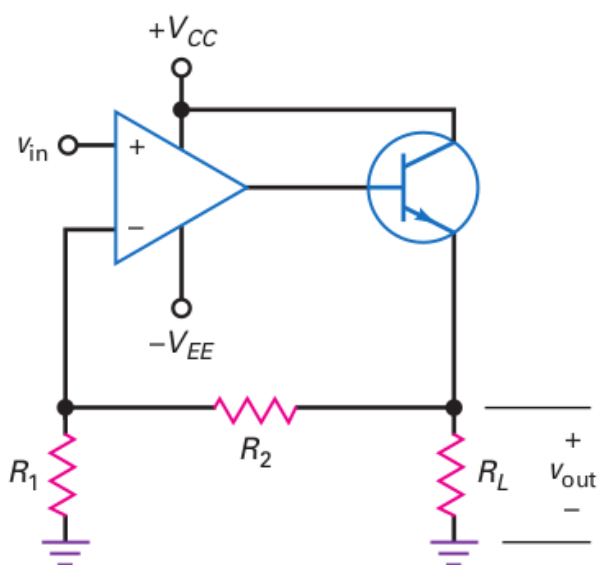**Q7.** Calculate the voltage gain and  $z_{out(CL)}$ . What is the purpose of the transistor



in this circuit?