

PH233

L1 (Mon) + L4 (Fri)

Session 0 – Orientation and Introduction to Opamps

PH233 (Electronics Lab – 2)

1. Will run in the same format as PH231. Monday + Friday afternoons
 - Monday: Lab of the week starts, concept discussion
 - Forum active. Submission Wednesday night,
Late submission (-30%) till Thursday night
 - Friday: Lab wrap-up + follow-up
2. **CONTENT: Everything is done with OPAMPS IC741 in your kit**
Please retain your astable multivibrator FG on your breadboard –
that will still serve as the FG for most experimental tests

Why Opamps?

Discrete Transistor circuits are not good enough, as voltage amplifier

VOLTAGE Amplifier: Want high gain, high input Z, low output Z


Limitation: R_C / emitter resistor sets gain

High $R_C \rightarrow$ High output Z



Low emitter resistor \rightarrow low input Z

Lab 4: Limited gain

CE amplifier Gain -10 (Lab 4)

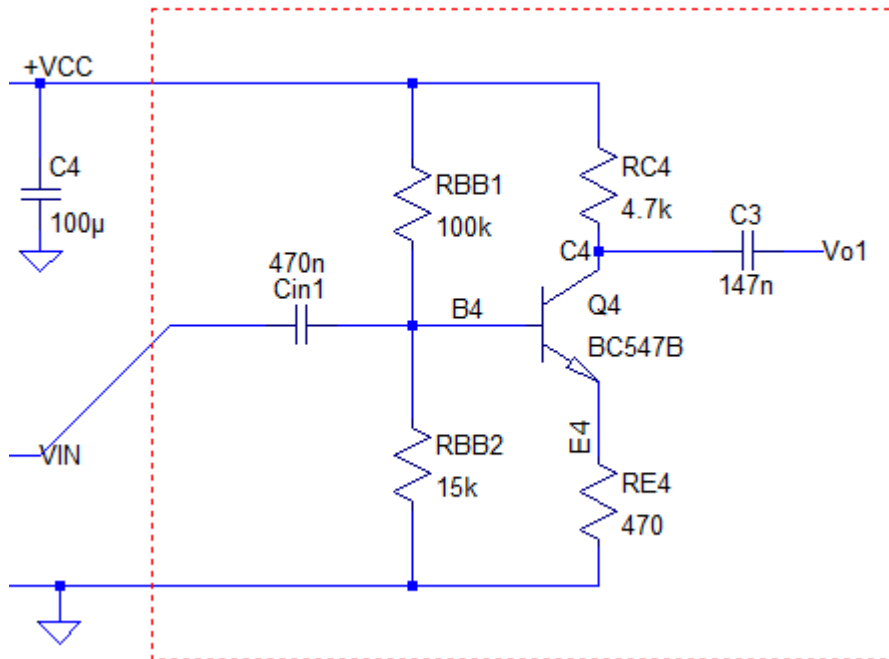


Endsem: High gain

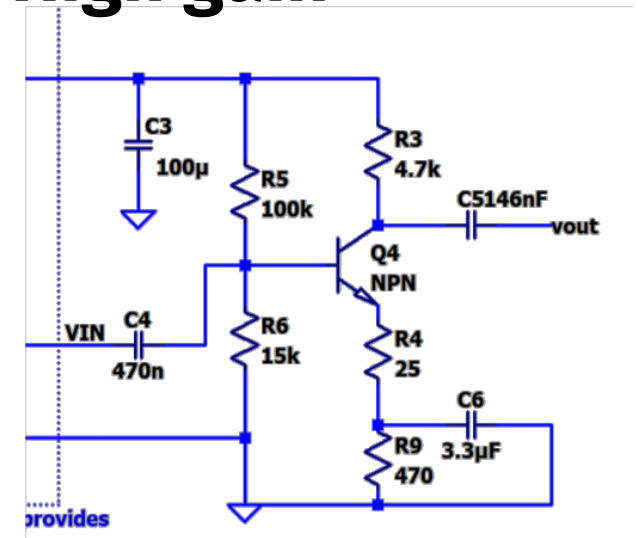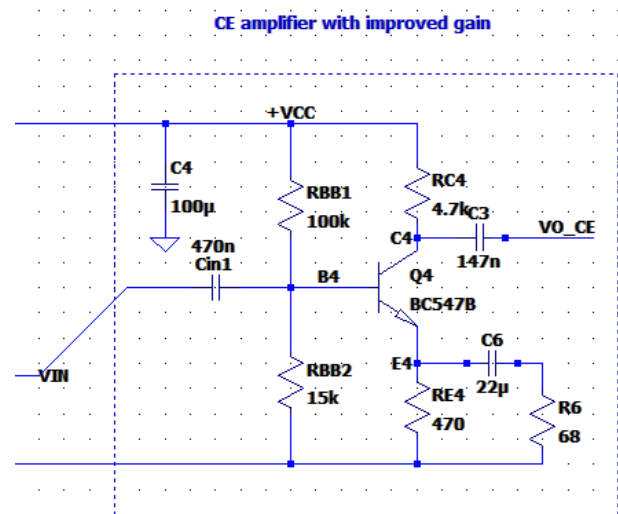

Discrete Transistor circuits are not good enough, as Current amplifier

Want: High Input Z, high Output Z

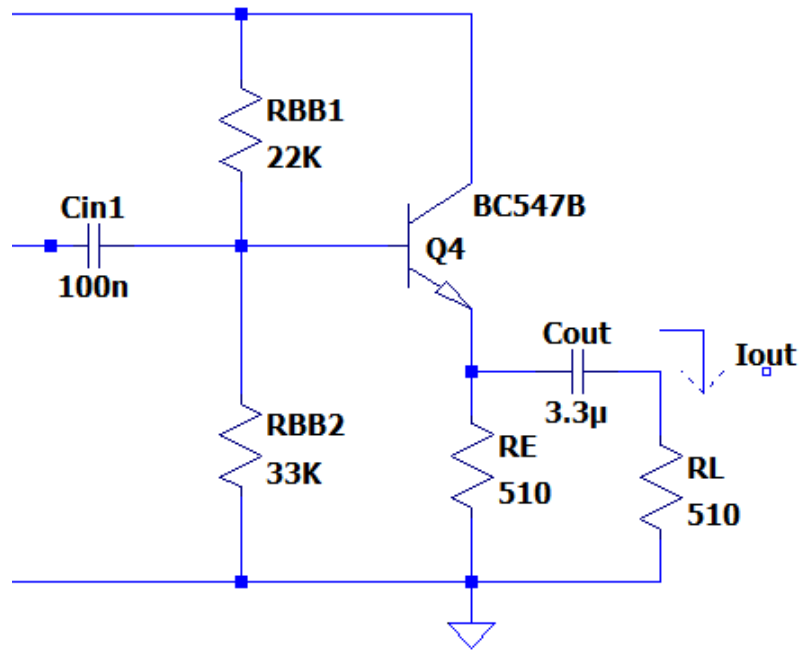


Limitation:

If we want high current gain,
need super high idle power dissipation
(recall efficiency is ~ 2%!)

R_E sets .op in middle of FA, must be low
So output Z and input Z are both low

General limitations of discrete transistor circuits we have not explored so far

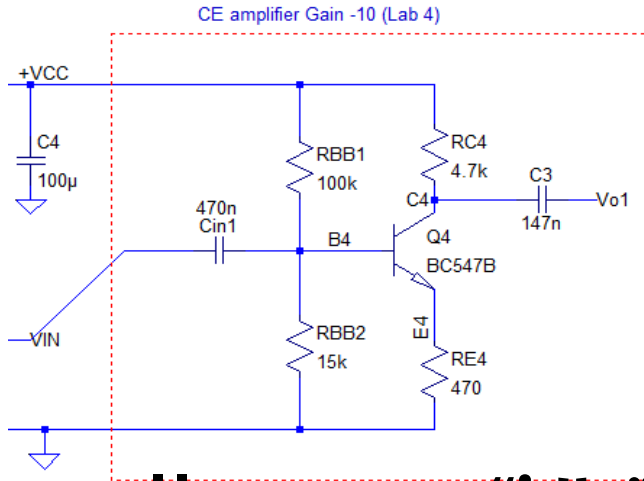


RBB1 || RBB2 are “idle” parts simply to set $V_B = V_E + 0.7$

RBB1, RBB2 value needs to be fine-tuned to keep $i_{b|DC}$ tiny – and they affect input impedance!


BETTER:

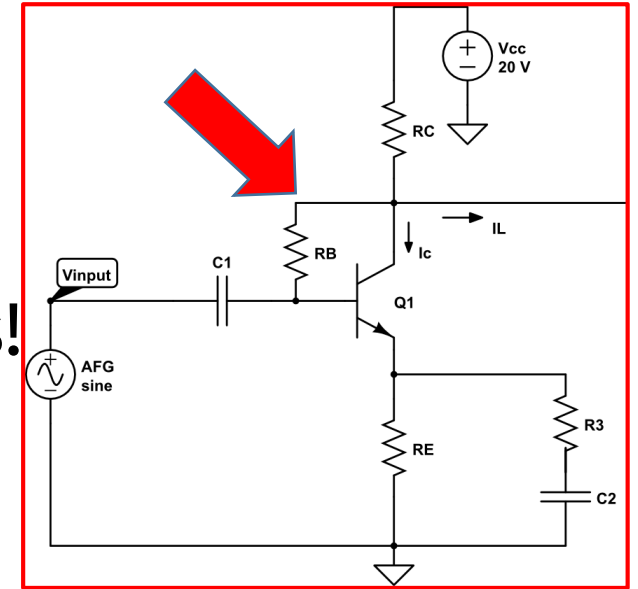R_B feedback from C to B stabilizes bias!




IDEALLY:

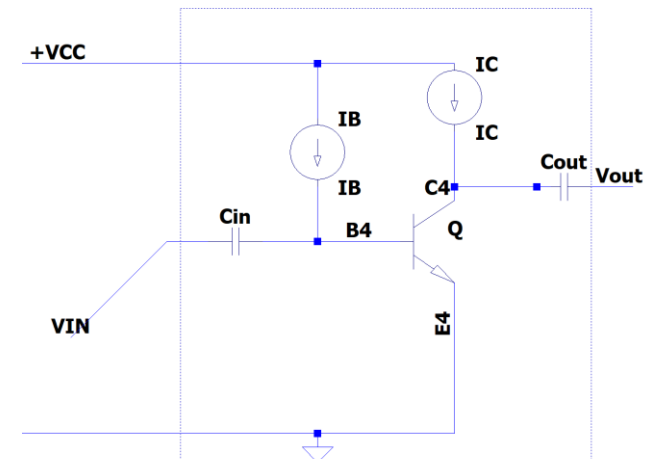
We want a current source supplying I_C, I_B V_E not dependent on r_e, R_E



OPAMP

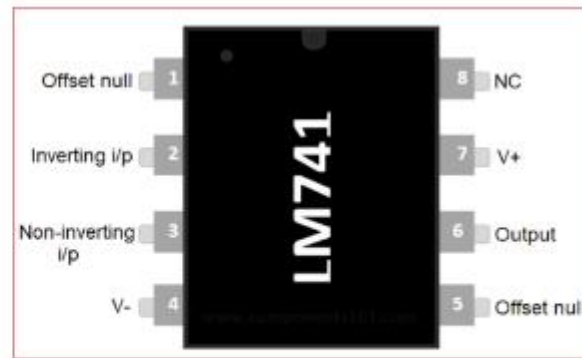

Typical Application

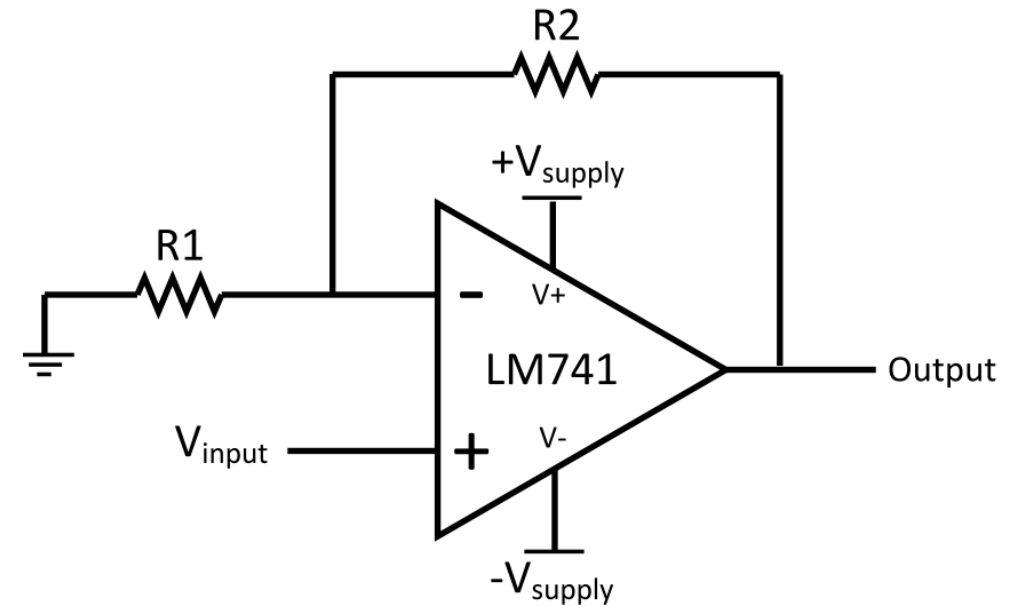


GAIN IS SET BY TWO EXTERNAL resistors $R1$, $R2$
No more calculating, fiddling with R_C , R_E , R_B !

WHAT'S INSIDE AN OPAMP?



V^- V^+


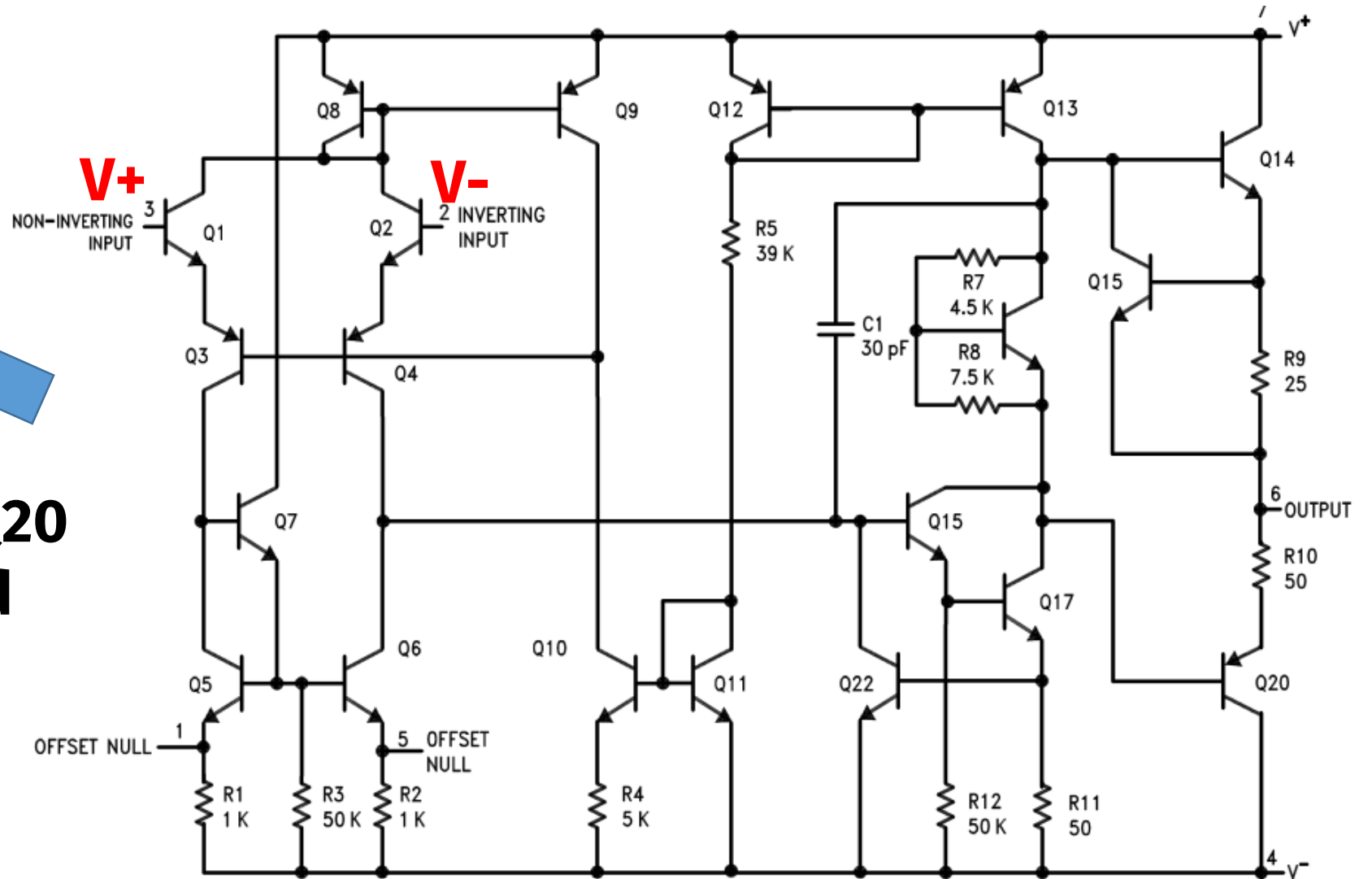
**ALL transistors Q1 – Q20
are precisely matched
and R values precise**



PRACTICAL ISSUES: HOW TO CONNECT AN OPAMP ON YOUR BREADBOARD


WITH RESPECT TO NOTCH ON IC

TOP LEFT PIN IS #1
THEN OTHER PINS ARE
COUNTER-CLOCKWISE

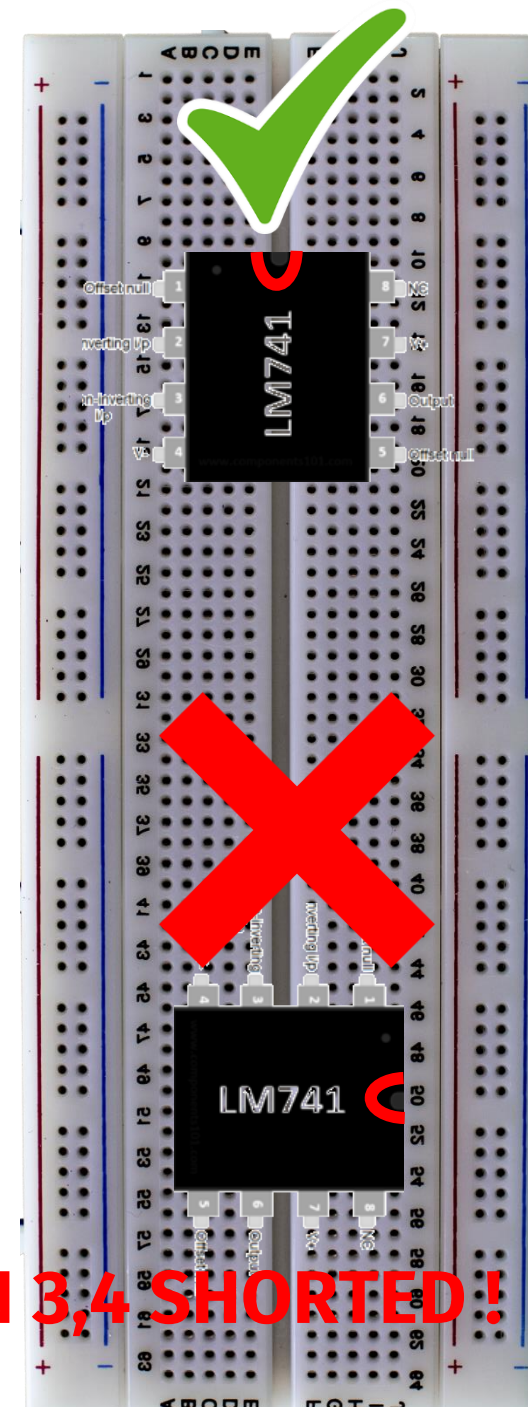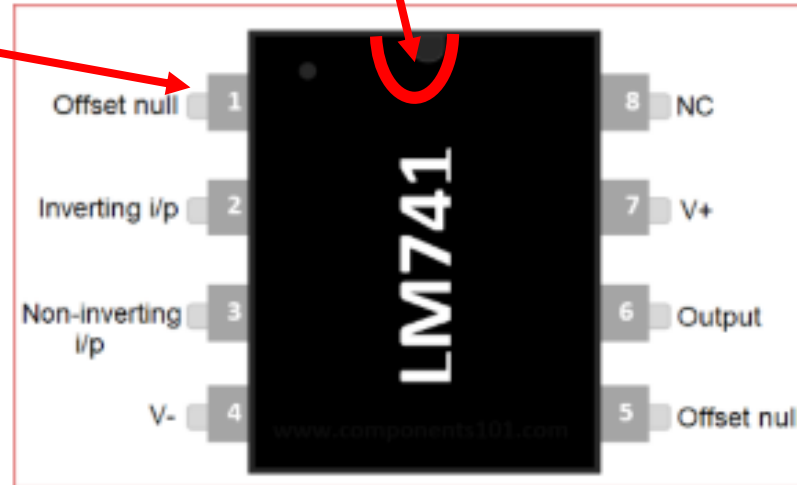

EXERCISE 1: WHAT ARE ALL THESE TRANSISTORS DOING??

INPUT
(differential)

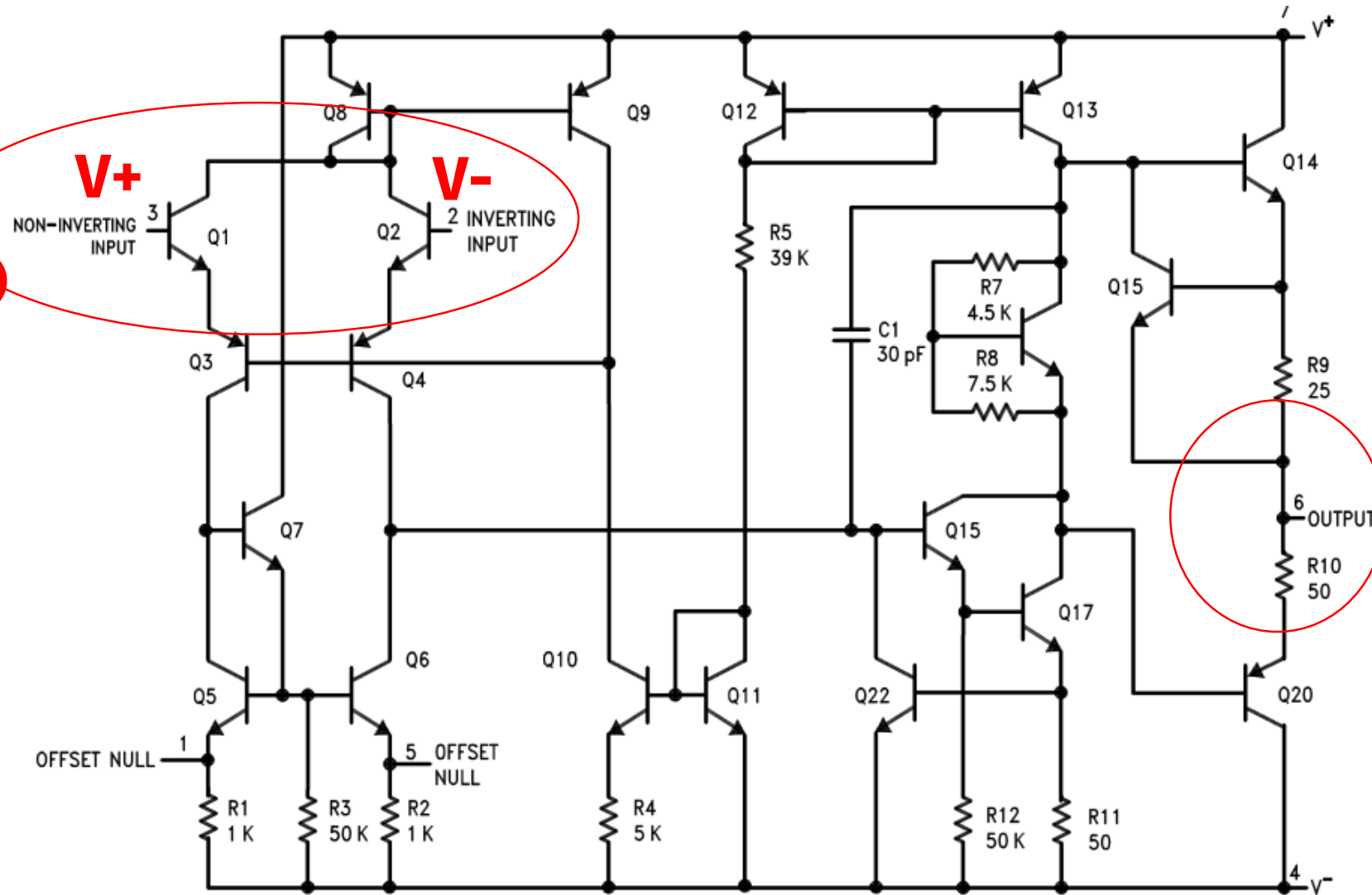

OUTPUT